



1

a. $P = \sqrt{3} \cdot V_{Lr,rms} \cdot I_{rms} \cdot \cos\phi$

$$10000 \text{ W} = \sqrt{3} \cdot V_{Lr,rms} \cdot \frac{3}{2} \cdot \frac{1}{\sqrt{2}} \cdot 30 \text{ A} \cdot 0,85$$



$$V_{Lr,rms} = \underline{\underline{213,46 \text{ V}}}$$

b. Diagram 2 is correct. The inductance in the motor gives a positive contribution to the phase angle of the current.

c. $\vec{B}_{int} = \mu_0 \cdot \frac{N_s}{2 \cdot l_g} \cdot \vec{i} = 4\pi \cdot 10^{-7} \cdot \frac{90}{2 \cdot 0,0015} \cdot \frac{3 \cdot 30 \text{ A}}{2} = \underline{\underline{1,6965 \text{ T}}}$

d. Number 2 is correct. Magnitude of B_{int} is twice that of B_{ad} and B_{cd} and both B_{ad} and B_{cd} are negative.



2

a Referencing V_{d-} to 0V and V_{d+} to 400V gives a voltage on A of 400V when $V_{id+} > V_{id-}$ and 0V if not.

~~$$R_A = \frac{400V \cdot 0,7 \cdot 0,35 \cdot 10^{-3} \cdot T}{400V \cdot T} = 0,7$$~~

~~The average voltage $\bar{U}_{AN} = 400V \cdot 0,7 = 280V$~~

$$R_A = \frac{V_{d+} \cdot 0,7 + V_{d-} \cdot (1-0,7)}{V_d} = \frac{400 \cdot 0,7 + 0 \cdot 0,3}{400} = \underline{\underline{0,7}}$$

$$\bar{U}_{AN} = V_d \cdot R_A = 400V \cdot 0,7 = \underline{\underline{280V}}$$

b $\bar{U}_{BN} = V_d \cdot (1-0,7) = 400 \cdot 0,3 = \underline{\underline{120V}}$

$$\bar{U}_0 = \bar{U}_{AN} - \bar{U}_{BN} = 280V - 120V = \underline{\underline{160V}}$$

c $\bar{U}_0 - \bar{I}_0 \cdot R_a - E_a = 0$

$$\frac{\bar{U}_0 - E_a}{R_a} = \bar{I}_0 = \frac{160V - 40V}{0,30 \Omega} = \underline{\underline{400A}}$$



$$2 \quad d \quad V_d - \bar{U}_d = L_d \cdot \frac{\Delta i_{o, \text{ripple}}}{\Delta t}$$

$$400V - 160V = 0,005H \cdot \frac{\Delta i_{o, \text{ripple}}}{0,7 \cdot 0,5 \cdot 10^{-4}s}$$

↓

$$\Delta i_{o, \text{ripple}} = \frac{400 - 160}{0,005} \cdot 0,7 \cdot 0,5 \cdot 10^{-4} = \underline{\underline{1,68A}}$$

e bipolar switching, thus $f_{\text{tri}} = f_{\text{out}}$.

$$f_{\text{tri}} = \frac{1}{0,5 \cdot 10^{-4}} = 20000 = \underline{\underline{20kHz}}$$

$$f_{\text{out}} = 20kHz$$

$$3 \quad a \quad \bar{V}_{ph} = \frac{\bar{V}_L}{\sqrt{3}} = \frac{460}{\sqrt{3}} = \underline{\underline{265,58V}}$$

$$\bar{V}_{TH} = \frac{j \cdot 18 \Omega}{0,58 \Omega + j \cdot 0,32 \Omega + j \cdot 18 \Omega} \cdot 265,58 = \underline{\underline{260,81V}} \quad (\text{eq. (6)})$$

$$Z_{TH} = \frac{j \cdot 18 \Omega \cdot (0,58 \Omega + j \cdot 0,32 \Omega)}{0,58 \Omega + j \cdot 0,32 \Omega + j \cdot 18 \Omega} = \underline{\underline{0,1505 \angle 30,70^\circ \Omega}}$$

$$R_{TH} = \text{Re}(Z_{TH}) = 0,15594 \Omega \quad X_{TH} = \text{Im}(Z_{TH}) = 0,3327 \Omega$$

$$n_{\text{sync}} = \frac{60 \cdot 60}{\frac{4}{2}} = 1800 \text{ rpm}$$

$$n_n = n_{\text{sync}} \cdot (1 - s) = 1800 \cdot \frac{100 - 3,5}{100} = \underline{\underline{1737 \text{ rpm}}}$$

$$\tilde{T}_{\text{ind}} = \tilde{T}_{\text{load}} = \frac{3 \cdot \frac{0,07}{0,035} \cdot 260,81^2}{1800 \cdot \frac{2\pi}{60} \cdot ((0,15594 + \frac{0,07}{0,035})^2 + (0,3327 + 0,3366)^2)} = \underline{\underline{30643 \text{ Nm}}} \quad (\text{eq. (8)})$$



$$3 \quad b \quad T_{\max} = \frac{3 \cdot 260,81^2}{2 \cdot 1800 \cdot \frac{2\pi}{60} \cdot (0,5594 + \sqrt{0,5594^2 + (0,3327 + 0,386)^2}} \\ = \underline{\underline{368,33 \text{ Nm}}} \quad (\text{eq (10)})$$

$$s_{x\max} = \frac{0,07}{-0,5594^2 + (0,3327 + 0,386)^2} = \underline{\underline{0,077}} \quad (\text{eq (9)})$$

$$n_{r\max} = n_{\text{sync}} \cdot (1 - 0,077) = \underline{\underline{1661,4 \text{ rpm}}}$$

c. The starting torque occurs when

$$n_{\text{slip}} = 0 \Rightarrow s_{\text{start}} = \underline{\underline{1}}$$

$$T_{\text{ind}(s=1)} = T_{\text{start}} = \frac{3 \cdot 0,07 \cdot 260,81^2}{1800 \cdot \frac{2\pi}{60} \cdot ((0,5594 + 0,07)^2 + (0,3327 + 0,386)^2)} \quad (\text{eq (8)})$$

$$T_{\text{start}} = \underline{\underline{83,77 \text{ Nm}}}$$

d. The motor corresponds with Nema class A due to a low start-up torque and a high torque close to synchronous speed.

A high R_2 increases the starting torque (torque at high slip). This corresponds with rotor 1. Our motor with a low starting torque corresponds with rotor 2.

The double cage rotor (3) achieves both high starting torque and nominal torque.

Rotor 1 - class D / Rotor 2 - class A / Rotor 3 - class C