



P1)

(i)

$$V_d = 12V \quad D = 0.6 \quad P_o = 36W \quad L = 25\mu H$$

$$\frac{V_o}{V_d} = \frac{D}{1-D} \quad \# \quad \frac{18V}{12V}$$

$$V_o = \frac{D}{1-D} V_d = \frac{0.6}{1-0.6} \times 12 = 18V$$


$$I_o = \frac{P_o}{V_o} = \frac{36}{18} = 2A$$

$$I_{in} = \frac{P_o}{V_{in}} = \frac{36}{12} = 3A$$

$$I_L = I_{in} + I_o = 2 + 3 = 5A$$

$$\Delta i_L = \frac{V_{in} D T_s}{L} = \frac{12 \times 0.6}{25 \times 10^{-6} \times 400 \times 10^3}$$

$$\Delta i_L = 0.72A$$

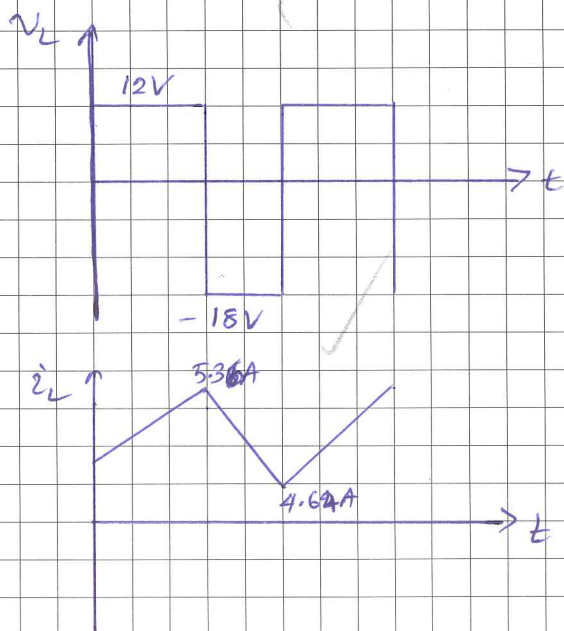

$$i_{Lmax} = I_L + \frac{\Delta i_L}{2}$$



$$= 5 + \frac{0.72}{2}$$

$$i_{Lmax} = \cancel{5.36A} \quad 5.36A$$

$$i_{Lmin} = I_L - \frac{\Delta i_L}{2}$$


$$= 5 - 0.36$$

$$i_{Lmin} = 4.64A$$

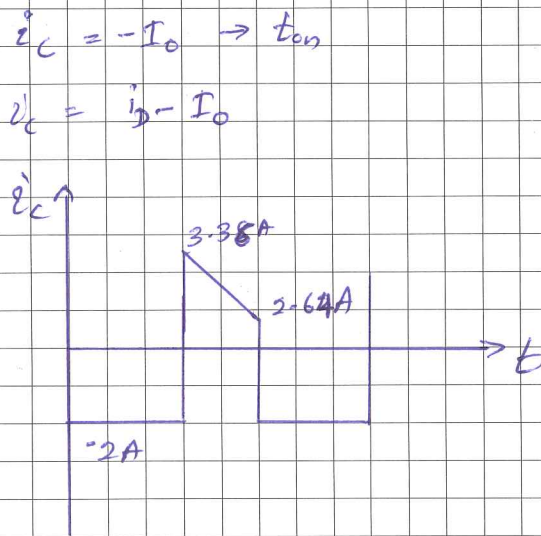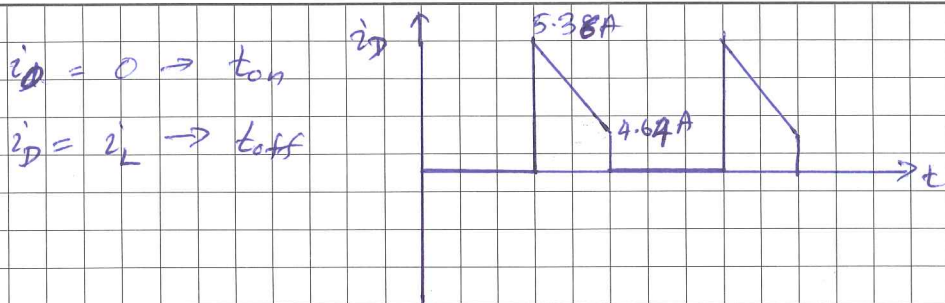

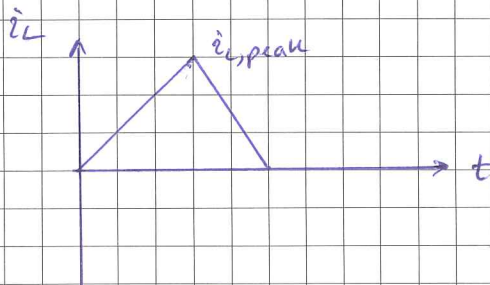(ii) At Critical conduction mode

$$i_{L,peak} = \frac{V_{in} D T_s}{L} \quad \left(\frac{V}{L \cdot \text{second}} \right)$$



$$I_{L,crit} = \frac{1}{2} \frac{V_{in} D T_s}{L}$$

$$I_{L,crit} = \frac{12 \times 0.6}{2 \times 25 \times 10^{-6} \times 400 \times 10^{-3}}$$

$$I_{L,crit} = 0.36 \text{ A}$$



$$I_L = I_{on} + I_o$$
$$= \frac{D I_o}{1-D} + I_o$$

$$I_L = \frac{I_o}{1-D}$$

$$\therefore I_o = I_L (1-D)$$

$$I_{o,crit} = 0.36 (1-0.6)$$

$$I_{o,crit} = 0.144 \text{ A}$$

$$P_o = V_o I_o =$$

$$P_{o,crit} = V_o I_{o,crit} = 18 \times 0.144$$

$$P_{o,crit} = 2.592 \text{ W}$$

Critical value
of P_o

(iii)

$$P_o = 5 \text{ W}$$

$$I_o = \frac{5}{18} = 0.278 \text{ A} = I_{o,crit}$$

$$I_{o,crit} = \frac{V_{in} D T_s}{2L} = \frac{V_o (1-D) T_s}{2L}$$

$$L_{crit} = \frac{V_o}{\left(\frac{I_{o,crit}}{1-D} \right)} \frac{(1-D) T_s}{2}$$



Emnekode : ENES05
Kandidatnr. : 212
Dato : 13/12/16
Ark nr. : 04 av 13

$$L_{crit} = \frac{V_0}{I_{crit}} \frac{(1-D)^2}{2f_s}$$
$$= \frac{18}{0.278} \times \frac{(1-0.6)^2}{2 \times 400 \times 10^3}$$
$$L_{crit} = \underline{\underline{12.96 \mu H}}$$



P2

22

For Buck Converter

$$V_o + \tilde{v}_o(t) = d(t) [V_{in} + \tilde{v}_{in}(t)]$$

$$V_o + \tilde{v}_o(t) = [D + \tilde{d}(t)] [V_{in} + \tilde{v}_{in}(t)]$$

$$V_o + \tilde{v}_o(t) = DV_{in} + D\tilde{v}_{in}(t) + \tilde{d}(t)V_{in} + \tilde{d}(t)\tilde{v}_{in}(t) \rightarrow 0$$


$$\tilde{v}_o(t) = D\tilde{v}_{in}(t) + \tilde{d}(t)V_{in}$$

$$I_{in} + \tilde{i}_{in}(t) = d(t) [I_o + \tilde{i}_o(t)]$$

$$I_{in} + \tilde{i}_{in}(t) = [D + \tilde{d}(t)] [I_o + \tilde{i}_o(t)]$$


$$I_{in} + \tilde{i}_{in}(t) = DI_o + D\tilde{i}_o(t) + \tilde{d}(t)I_o + \tilde{d}(t)\tilde{i}_o(t) \rightarrow 0$$
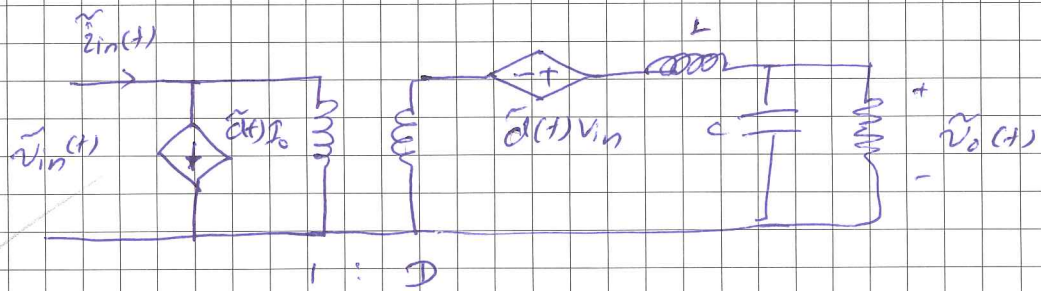
$$\tilde{i}_{in}(t) = D\tilde{i}_o(t) + \tilde{d}(t)I_o$$




small signal perturbation at

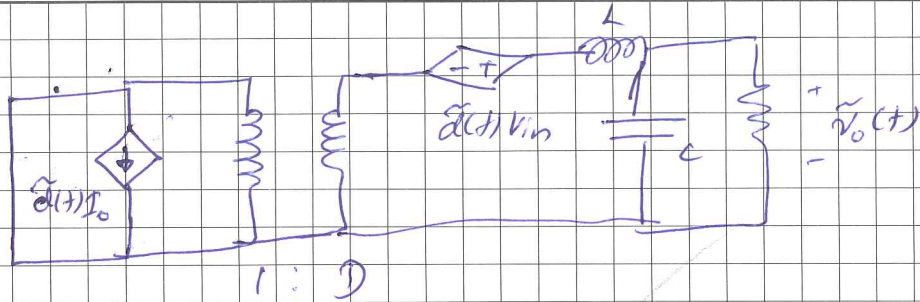Considering steady state operating condition
 $\tilde{v}_{in}(t) = 0$



2.1

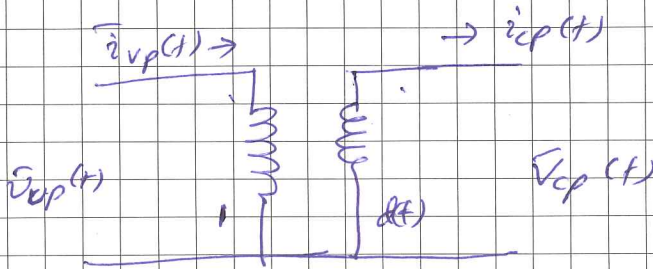

$$\tilde{v}_{cp} = d(t) \tilde{v}_{vp}$$


$$\tilde{v}_{cp} + \tilde{v}_{cp}(t) = [D + d(t)] [V_{vp} + \tilde{v}_{vp}(t)]$$

$$\tilde{v}_{cp}(t) = D \tilde{v}_{vp} + d(t) V_{vp}$$

$$\tilde{i}_{cp}(t) = d(t) \tilde{i}_{cp}(t)$$

$$I_{vp} + \tilde{v}_{vp}(t) = [D + d(t)] [I_{cp} + \tilde{i}_{cp}(t)]$$
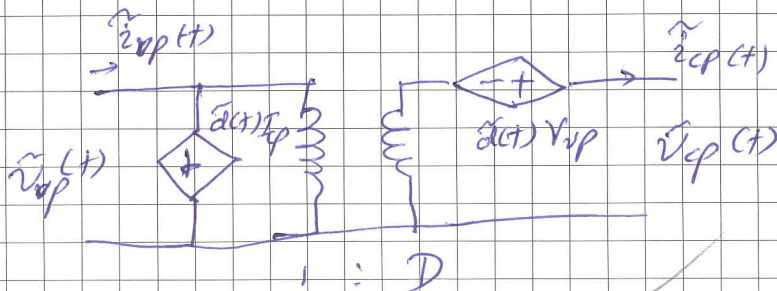
$$\tilde{i}_{vp}(t) = D \tilde{i}_{cp}(t) + d(t) I_{cp}$$





P3

3.1

$$I_s = 10 A_{\text{rms}} \quad I_{s1} = 8 A_{\text{rms}} \quad \text{DPF} = 0.85$$

$$(a) \quad I_s = \sqrt{I_{s1}^2 + I_{\text{dis}}^2}$$

~~I_{dis}~~

$$I_{\text{dis}} = \sqrt{I_s^2 - I_{s1}^2}$$

$$= \sqrt{10^2 - 8^2}$$

$$I_{\text{dis}} = 6 A$$

$$(b) \quad \text{THD \%} = \frac{I_{\text{dis}} \times 100\%}{I_{s1}}$$

$$= \frac{6}{8} \times 100\%$$

$$= 75\%$$

$$(c) \quad \text{PF} = \frac{I_{s1}}{I_s} \cdot \text{DPF}$$

$$= \frac{8}{10} \times 0.85$$


$$\text{PF} = 0.68$$

The THD is equal to 75%. It is a higher range of distortion. It causes the system to have



a low power factor. Need a Power factor Correction system

3-2

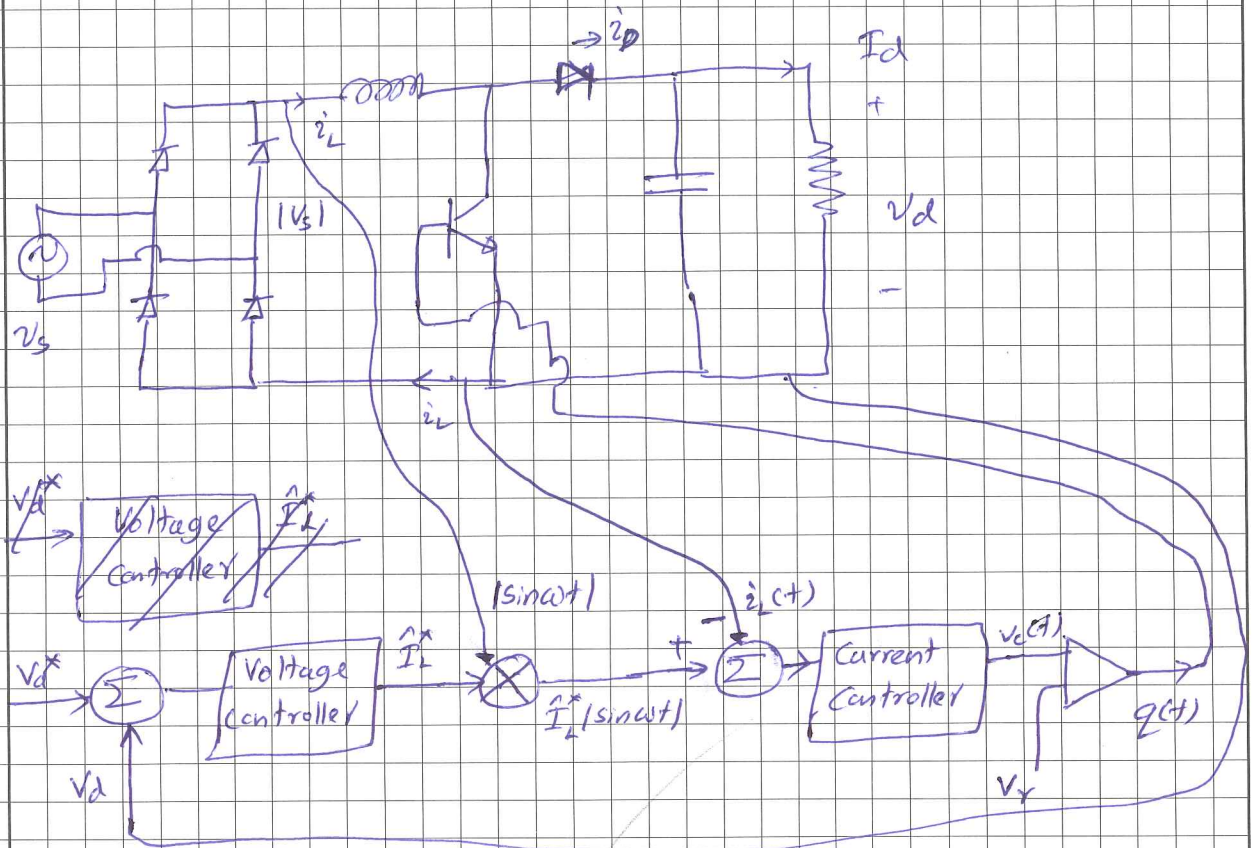

The average inner current controller loop ensures the form $i_L^*(t)$ based on the template $|\sin \omega t|$ measured from $|V_s|$ of the voltage rectifier bridge. A control voltage $v_c(t)$ is generated and it compared with a ramp signal v_r to generate a switching signal for boost converter switch.

The voltage control loop determines the peak amplitude of \hat{i}_L^* of inductor current based on O/P voltage feedback. If inductor current is insufficient for a given load supplied by PFC, the O/P



Emnekode : ENE505
Kandidatnr. : 212
Dato : 13/2/16
Ark nr. : 09 av 13

voltage drops below its preselected reference value. By measuring op voltage & using it as feedback signal, voltage controller adjust the induct current amplitude to maintain op voltage at reference value V_d .

Voltage controller acts to regulate op voltage to reference value V_d in addition to determine the inductor peak amplitude.



P4

A.1

$$V_{in} = V_s = 120 V_{rms} \quad f = 60 \text{ Hz}$$

$$V_d = 250 \text{ V} \quad P_o = 300 \text{ W}$$

lossless ac-f

$$\frac{|V_d|}{|V_s|} = \frac{1}{1-d(t)}$$

$$I_s = \frac{P_o}{V_s}$$

$$I_s = \frac{300}{120} = 2.5 \text{ A}$$

$$1-d(t) = \frac{|V_s|}{|V_d|}$$

~~$$i_L = \sqrt{2} \times 2.5 \sin(120\pi t)$$~~


~~$$i_L = 2.5 \sqrt{2} \sin(120\pi t)$$~~

$$i_L = 2.5 \sqrt{2} |\sin(120\pi t)|$$

$$d(t) = 1 - \frac{|V_s|}{V_d}$$

$$d(t) = 1 - \frac{\sqrt{2} \times 120 |\sin(2\pi \times 60)t|}{250}$$

$$d(t) = 1 - 0.68 \sin((120\pi)t)$$

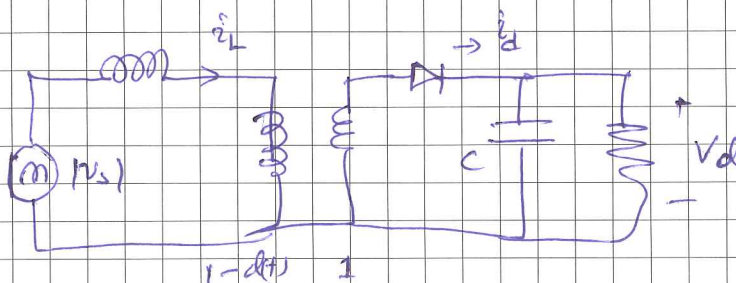

$$i_d(t) = [1-d(t)] i_L(t)$$

$$= \frac{|V_s|}{V_d} \cdot |I_s| = \frac{\sqrt{2} I_s}{V_d} \sin^2 \omega t$$



$$i_d(t) = \frac{1}{2} \frac{\hat{V}_{in} \hat{I}_L}{V_d} - \frac{1}{2} \frac{\hat{V}_{in} \hat{I}_L^n}{V_d} \cos 2\omega t$$



$$= \frac{1}{2} \times \frac{120\sqrt{2} \times 25\sqrt{2}}{250} - \frac{1}{2} \frac{120\sqrt{2} \times 25\sqrt{2}}{250} \cos(4\pi \times 60)t$$

$$i_d(t) = \frac{1.2}{2} - 1.2 \cos(240\pi)t$$


i_{d2} - capacitor current

load current = 1.2 A

Capacitor Current = 1.2 cos 2ωt

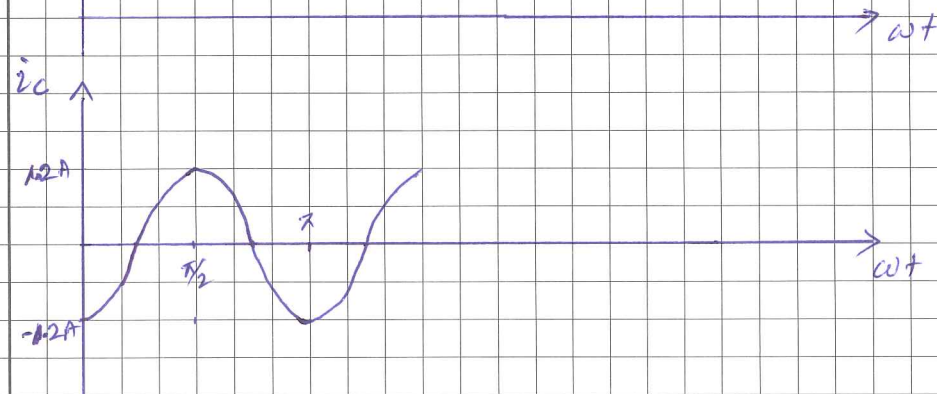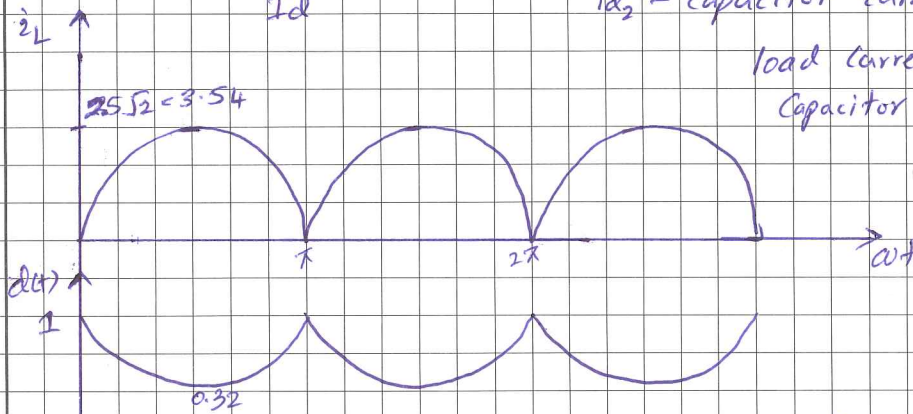

4.2

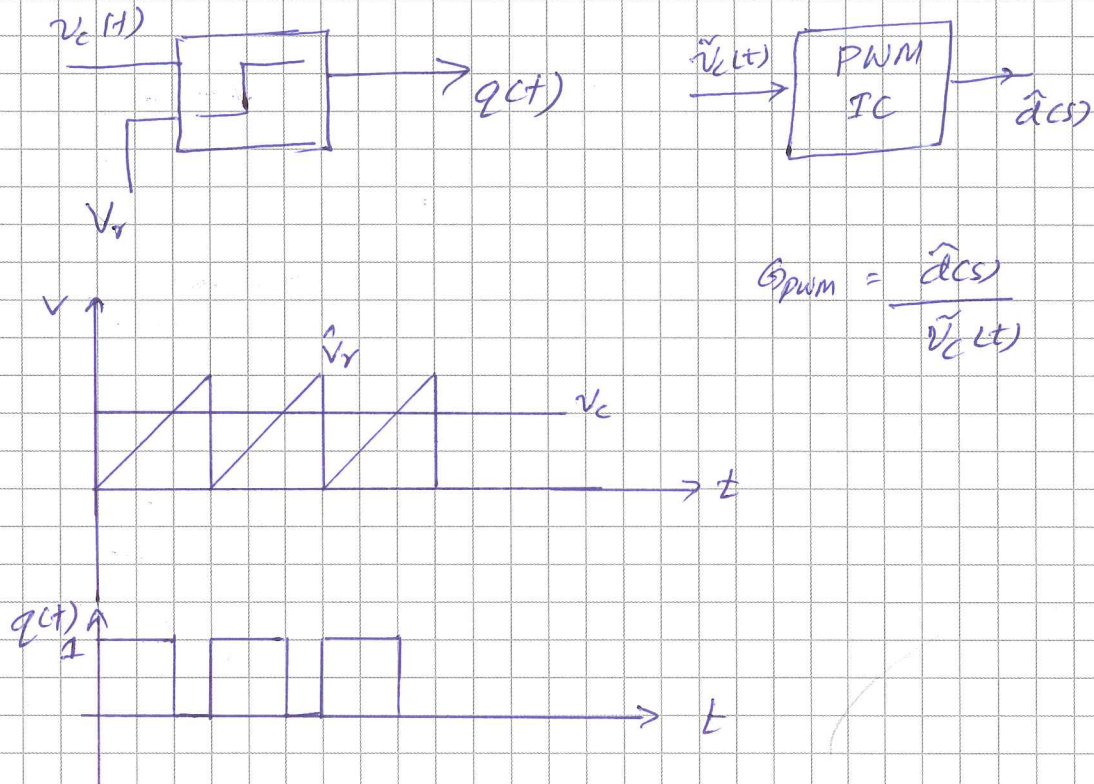

$$G_{pwm} = \frac{\hat{i}_{dcs}}{\tilde{v}_c(t)}$$

The control voltage $v_c(t)$ is generated by the error amplifier and compared with a ramp signal

$$v_c(t) = V_c + \tilde{v}_c(t)$$

The o/p switching signal is represented by $q(t)$ which is equal to 1, if $v_c(t) \geq V_r$, otherwise 0. The duty ratio of switch signal is defined as below

$$\frac{v_c(t)}{\hat{V}_r} = \frac{V_c}{\hat{V}_r} + \frac{\tilde{v}_c(t)}{\hat{V}_r}$$

$$\downarrow$$

$$d(t) = D + \tilde{d}(t)$$

$$\tilde{d}(t) = \frac{\tilde{v}_c(t)}{\hat{V}_r}$$



Emnekode : ENE505
Kandidatnr. : 212
Dato : 13/12/2016
Ark nr. : 13 av 13

$$\tilde{d}(s) = \frac{\tilde{v}_c(s)}{\hat{v}_r}$$

$$|G_{pwm}(s)| = \frac{\tilde{d}(s)}{\tilde{v}_c(s)} = \frac{1}{\hat{v}_r}$$